

EE671: VLSI Design

Assignment No. 2

Dikshit Singla, 23B3974
August 27, 2024

Q1) Minimum Size CMOS Inverter Design

Layout

 


Figure 1: Layout of Strength 1 Inverter

The layout has a total width of $2.72\mu\text{m}$, as shown in the figure. Please note that in the top left corner DRC check is 0.

Layout Versus Schematic

```
Class: sg13_lv_pmos      instances: 1
Class: sg13_lv_nmos      instances: 1
Circuit contains 4 nets.
Contents of circuit 2: Circuit: 'not1'
Circuit not1 contains 2 device instances.
Class: skyl30_fd_pr__nfet_0lv8 instances: 1
Class: skyl30_fd_pr__pfet_0lv8 instances: 1
Circuit contains 4 nets.

Circuit 1 contains 2 devices, Circuit 2 contains 2 devices.
Circuit 1 contains 4 nets, Circuit 2 contains 4 nets.

Final result:
Netlists do not match.
Port matching may fail to disambiguate symmetries.
Logging to file "comp.out" disabled
LVS Done.
/foss/designs >
```

Figure 2: LVS Check of Strength 1 Inverter

The LVS check confirmed that the circuits aren't match uniquely due to the difference in area and perimeter otherwise rest of the things were fine.

Simulation Results

I got the pex file which contain the subckt but it is not giving result in spice

Q2) Strength-2 Inverter Design (INVX2)

Layout

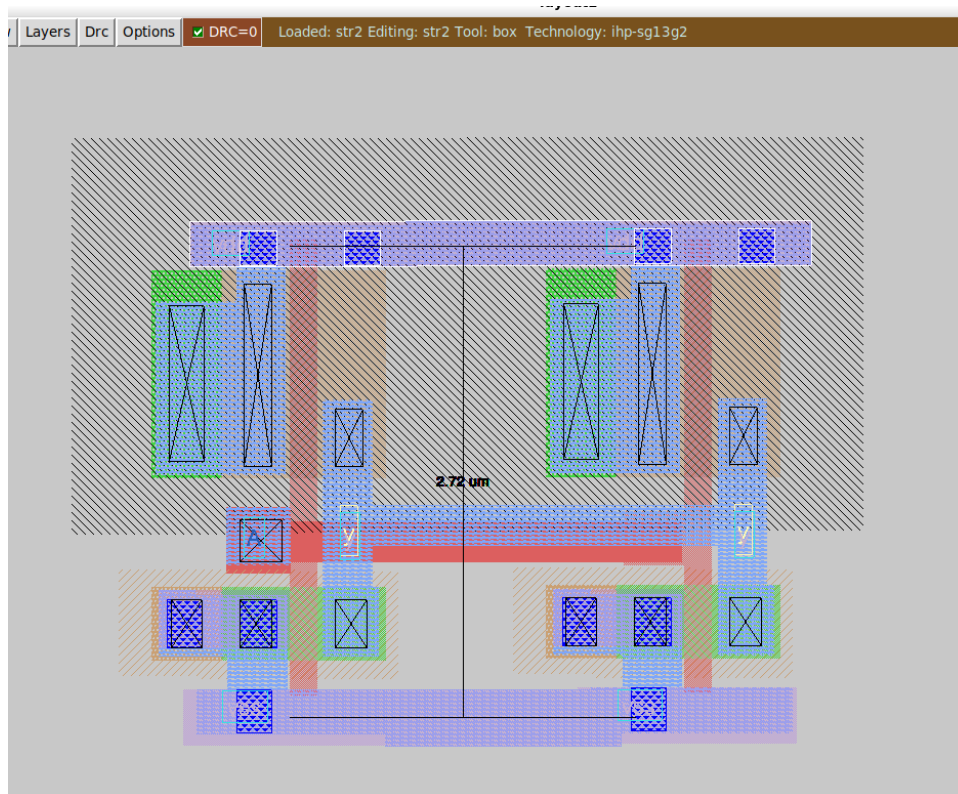


Figure 3: Layout of Strength 2 Inverter

The layout has a total width of $2.72\mu\text{m}$, as shown in the figure. Please note that in the top left corner DRC check is 0.

The DRC check was performed, and no errors were found.

Layout Versus Schematic

```

4 = 2
Instance: sg13_lv_pmos:1
  1 = 2
  2 = 2
  3 = 2
  4 = 2
-----
Netlists do not match.
Port matching may fail to disambiguate symmetries.

Subcircuit pins:
Circuit 1: assgn2_trial
vdd
vss
a_n10_n92#
y
-----
Cell pin lists for assgn2_trial and not1 altered to match.
Device classes assgn2_trial and not1 are equivalent.

Instance: sky130_fd_pr_pfet_01v
  (1,3) = (2,2)
  2 = 2
  4 = 2
-----
Circuit 2: not1
vdd
vss
|A **Mismatch**
|y
-----
Logging to file "comp.out" enabled
Contents of circuit 1: Circuit: 'assgn2_trial'
Circuit assgn2_trial contains 2 device instances.
  Class: sg13_lv_pmos instances: 1
  Class: sg13_lv_nmos instances: 1
Circuit contains 4 nets.
Contents of circuit 2: Circuit: 'not1'
Circuit not1 contains 2 device instances.
  Class: sky130_fd_pr_nfet_01v8 instances: 1
  Class: sky130_fd_pr_pfet_01v8 instances: 1
Circuit contains 4 nets.

Circuit 1 contains 2 devices, Circuit 2 contains 2 de
Circuit 1 contains 4 nets, Circuit 2 contains 4 ne

Final result:
Top level cell failed pin matching.
Logging to file "comp.out" disabled
LVS Done.
/foss/designs >

```

Figure 4: LVS Check of Strength 2 Inverter

The LVS check confirmed that input port is not matching.

Simulation Results

I got the pex file which contain the subckt but it is not giving result in spice
I have attached pex files and layout.spice files