

EE671 – VLSI Design

Assignment 3: 16-bit Kogge-Stone Adder – Synthesis Report

Group: 28
Course: EE671 – VLSI DESIGN
Submitted by: Dikshit Singla(23b3974)
Mohammad Bohra(25M1254)
Sahil Wani(23b3945)

October 6, 2025

Abstract

This report documents the design, verification (pre- and post-synthesis), synthesis results, and the RTL/netlist outputs for a 16-bit Kogge–Stone (KS) adder. The design follows the lab instructions for a register-input, registered-output adder with clocked input registers and clocked output registers. Screenshots and synthesis metrics from Cadence Genus are included.

1 Introduction

The objective of this assignment was to design a 16-bit Kogge–Stone tree adder, verify it using a testbench, and synthesize the design using Cadence Genus to produce the RTL gate-level netlist and reports. The module interface is:

- **Inputs:** A[15:0], B[15:0], CIN, CLK, RST_N (active low)
- **Outputs:** SUM[15:0], COUT

2 Design Description

1. The adder is implemented as a Kogge–Stone parallel-prefix carry network for fast carry propagation.
2. Inputs A, B, and CIN are sampled into input registers on the rising edge of CLK. The adder computes SUM and COUT combinationally and these are registered at the output on the next rising edge of CLK.
3. All modules and top-level files are written in Verilog with appropriate comments and indentation.

3 Pre-synthesis Verification

3.1 Simulation Setup

- Simulator: Icarus (iverilog) / gtkwave for waveform inspection.
- Testbench: Stimulates multiple vectors including carry propagation edge cases (all-0s, all-1s, alternating patterns, random vectors).
- Clock: 100 MHz (as per assignment).

3.2 Pre-synthesis Waveform

 


Figure 1: Pre-synthesis simulation waveform (replace `figures/pre_synthesis_waveform.png` with your `waveforms.vcd` screenshot).

4 Synthesis

Synthesis was performed with Cadence Genus using provided `synthesis.tcl` and constraints (`constraints.sdc`). Target clock: 100 MHz.

4.1 Area and Summary Report


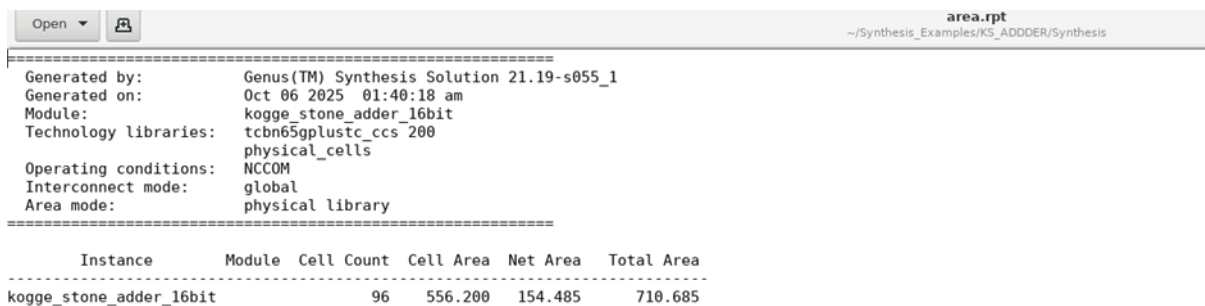


Figure 2: Screenshot of the area report after synthesis

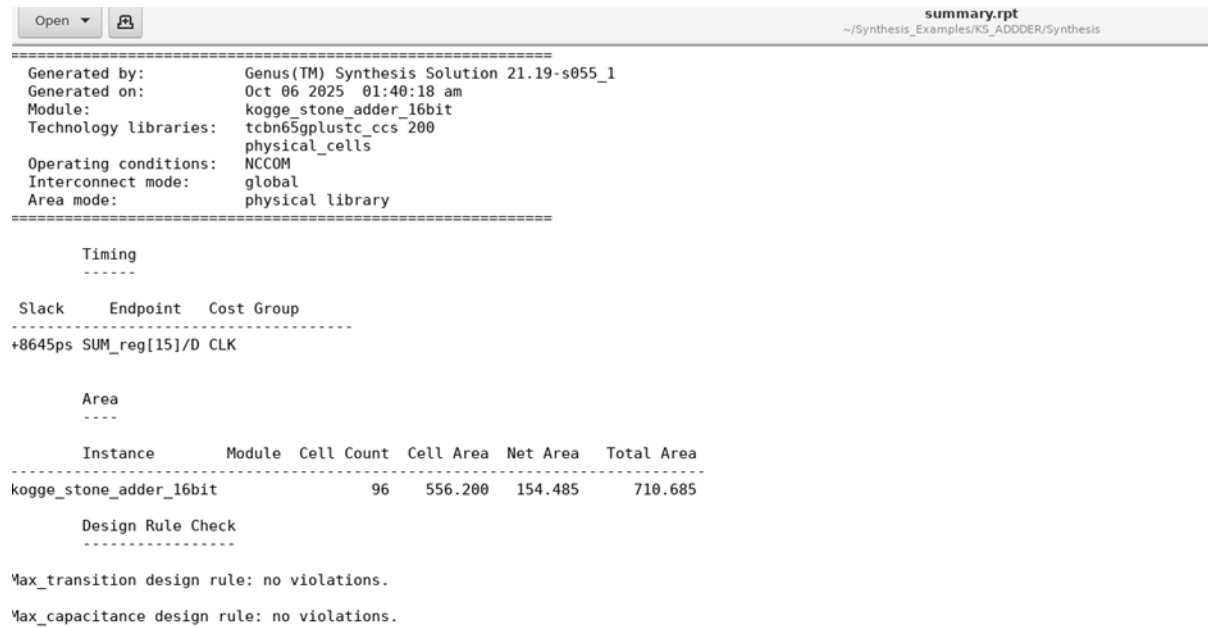

```

=====
Open  [icon] summary.rpt
~/Synthesis_Examples/KS_ADDDER/Synthesis
=====
Generated by: Genus(TM) Synthesis Solution 21.19-s055_1
Generated on: Oct 06 2025 01:40:18 am
Module: kogge_stone_adder_16bit
Technology libraries: tcbn65gplustc_ccs 200
                    physical_cells
Operating conditions: NCCOM
Interconnect mode: global
Area mode: physical library
=====

Timing
-----

Slack      Endpoint      Cost Group
-----
+8645ps SUM_reg[15]/D CLK

Area
----

Instance      Module  Cell Count  Cell Area  Net Area  Total Area
-----
kogge_stone_adder_16bit      96    556.200    154.485    710.685

Design Rule Check
-----

Max_transition design rule: no violations.
Max_capacitance design rule: no violations.

```

Figure 3: Screenshot of the summary report after synthesis

4.2 Cell Count Summary

Table 1: Cell summary

Description	Count (example)
Number of combinational cells	46
Number of sequential cells (flip-flops)	50
Total number of cells	96

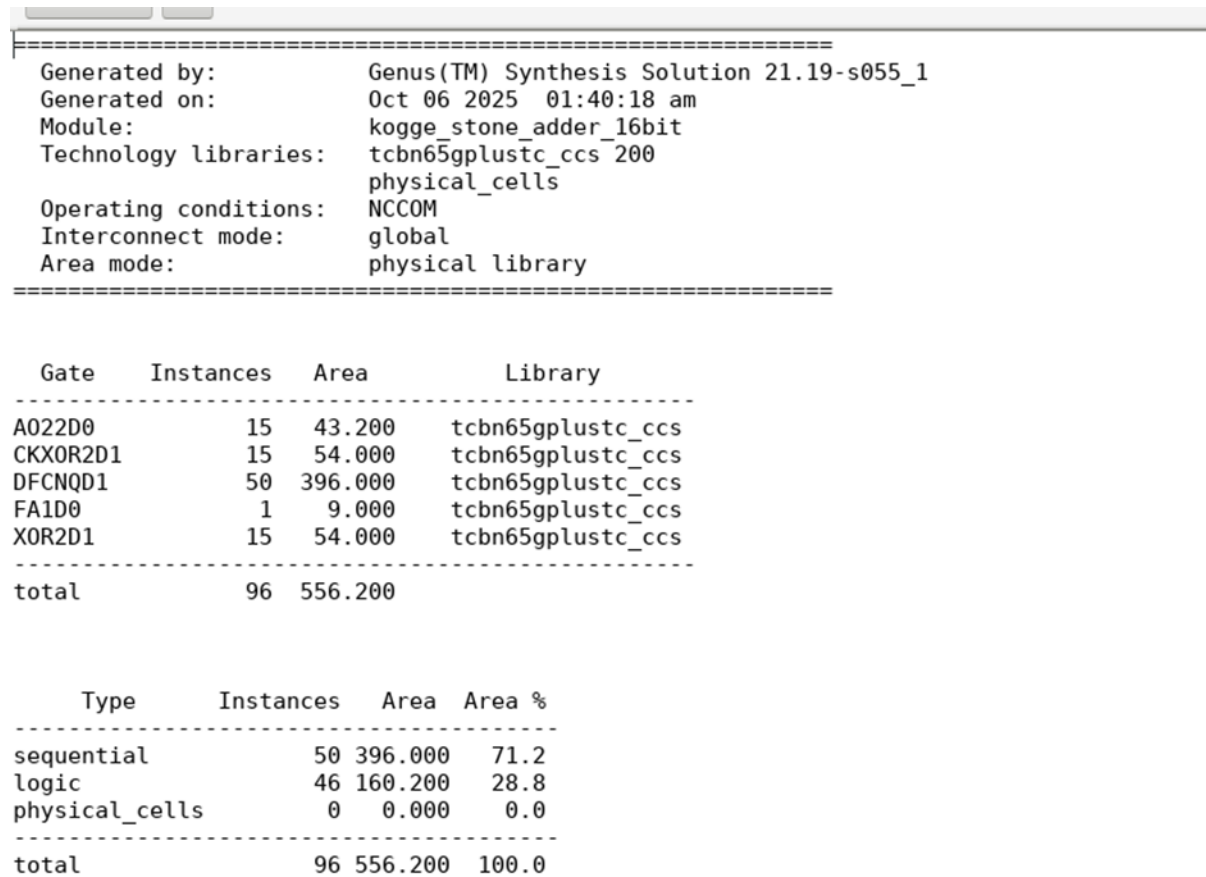


Figure 4: Results

5 Post-synthesis Verification



Figure 5: Post-synthesis (gate-level) simulation waveform

6 Files Submitted (ZIP)

1. KSadder.v – Top-level Verilog source .
2. KSadder_TB.v – Testbench file
3. KS_adder_netlist.v – Post-synthesis RTL netlist (from Genus).

7 Conclusion

The 16-bit Kogge–Stone adder was implemented, verified (pre- and post-synthesis), and synthesized. Post-synthesis functional verification confirms equivalence with pre-synthesis behavior (replace with formal equivalence / comparison summary if available). The RTL netlist and synthesis reports are included in the submission ZIP.
